


Universal Gates

- ◇ **The gate can be used to replace an AND gate, an OR gate, or an INVERTER gate.**
- ◇ **1. NAND Gate**
- ◇ **2. NOR Gate**

Universal Gate - NAND


- ◇ **NAND is the contraction of AND & NOT gates.**
- ◇ **it has two or more inputs and only one output i.e. $Y = (A \cdot B)'$**
- ◇ **When all the inputs are HIGH, the output is LOW. If any one or both the inputs are LOW, then the output is HIGH.**

NAND Gate

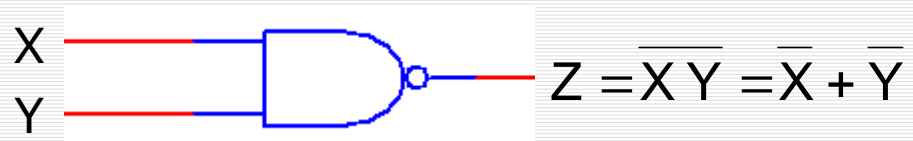

X	Y	Z
0	0	1
0	1	1
1	0	1
1	1	0


NAND Gate as an Inverter (NOT) Gate

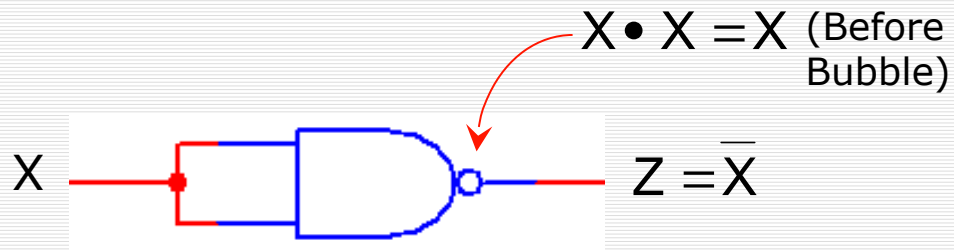

X	Z
0	1
1	0

Equivalent to Inverter


NAND Gate as an AND Gate

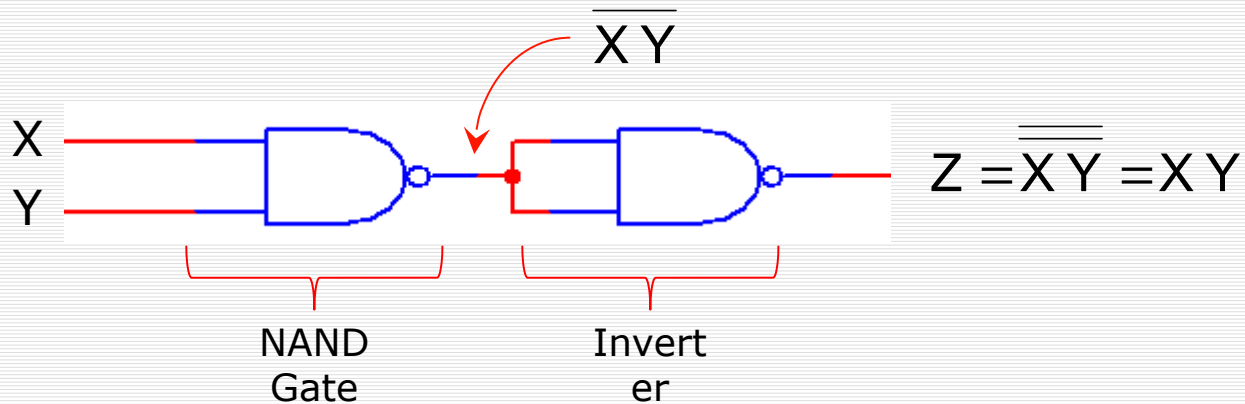

X	Y	Z
0	0	0
0	1	0
1	0	0
1	1	1

Equivalent to AND Gate


NAND Gate as an OR Gate

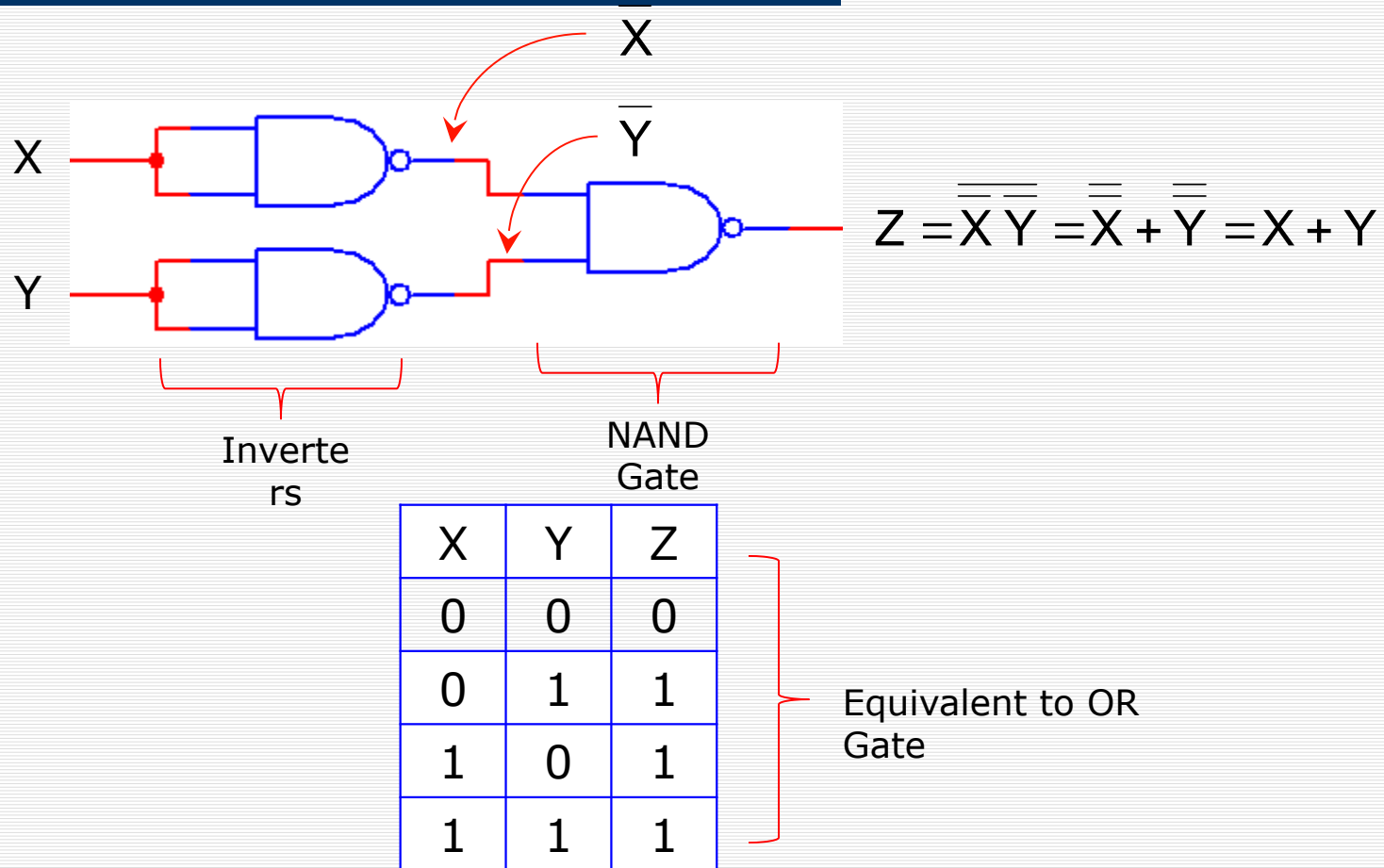

Universal Gate - NOR


- ◇ **NOR gate is the contraction of OR & NOT gates.**
- ◇ **NOR gate can be using to replace an AND gate, an OR gate or an INVERTER gate.**

NOR Gate

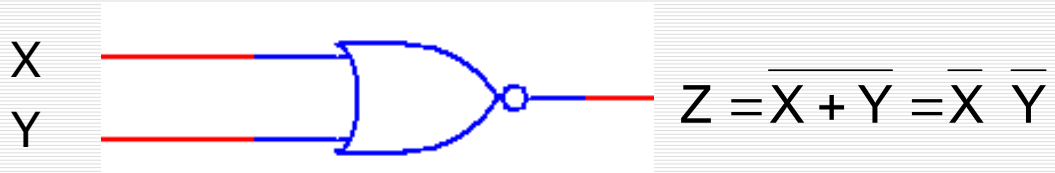

X	Y	Z
0	0	1
0	1	0
1	0	0
1	1	0


NOR Gate as an Inverter (NOT) Gate

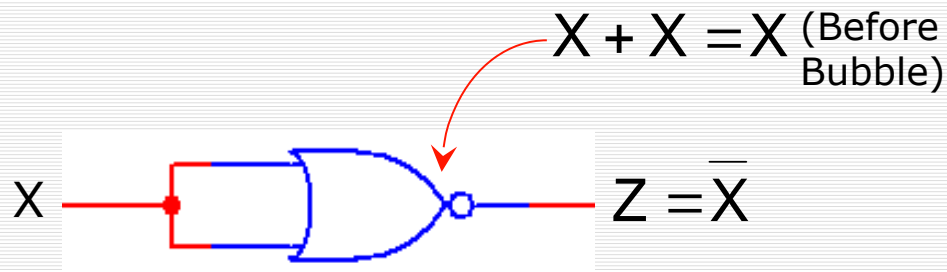

X	Z
0	1
1	0

Equivalent to Inverter


NOR Gate as an OR Gate

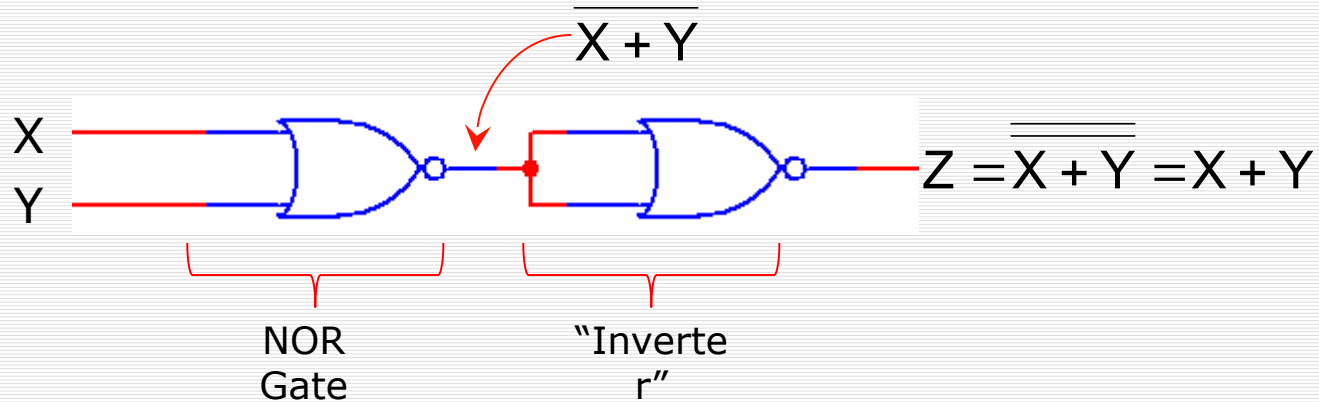

X	Y	Z
0	0	0
0	1	1
1	0	1
1	1	1

Equivalent to OR Gate

NOR Gate as an AND Gate

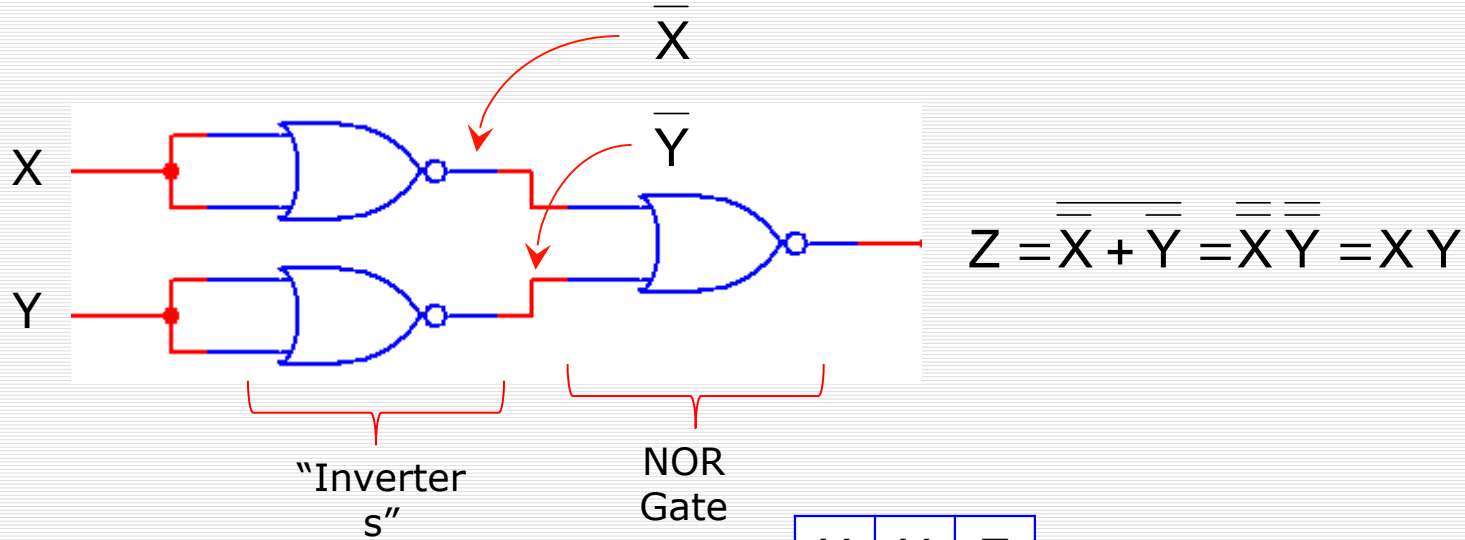

X	Y	Z
0	0	0
0	1	0
1	0	0
1	1	1

Equivalent to AND Gate