

104. Computer Organization

Unit – 3

Gates and Boolean Algebra

Digital Signals

- ◇ **Digital Signals have two basic states:**
 - 1 (logic "high", or H, or "on")
 - 0 (logic "low", or L, or "off")
- ◇ **Digital values are in a *binary* format. Binary means 2 states.**
- ◇ **A good example of binary is a light (only on or off)**



ON

Logic Gates

- ◇ **A logic gate is an electronic circuit which implements logical operation produces a typical output signal depending on its input signal.**
- ◇ **Binary information is represented in digital computers using electrical signals**

-
- ◇ **Logic circuits are built from components called logic gates.**
 - ◇ **The logic gates correspond to Boolean operations $+$, $*$, $'$.**
 - ◇ **Binary operations have two inputs, unary has one**

Digital Logic


- ◇ **Basic Digital logic is based on 3 primary functions (the basic gates):**
 - ◇ **AND**
 - ◇ **OR**
 - ◇ **NOT**

The AND Gate

- ◇ **The AND function:**
 - ◇ **If all the inputs are high , the output is high**
 - ◇ **If any input is low, the output is low**

AND Logic Symbol


Boolean Function : $F = AB$

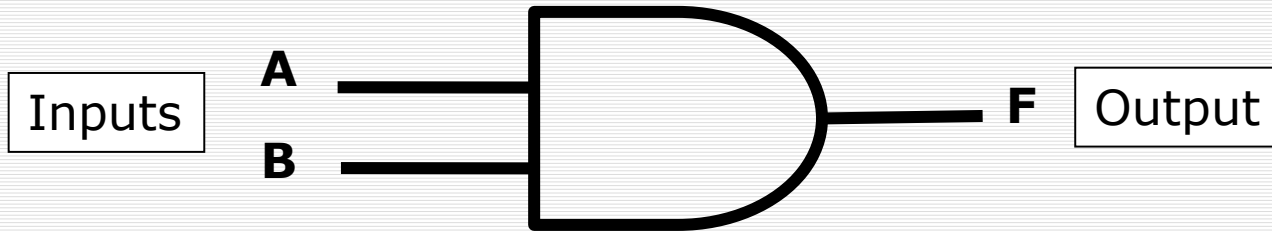

If all inputs are 1, the output is 1


If any input is 0, the output is 0

AND Logic Symbol

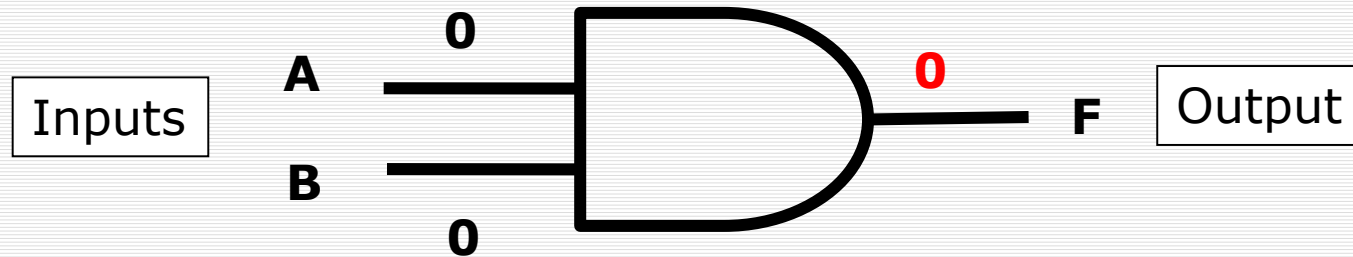

$$\begin{aligned}\text{Boolean Function : } F &= AB \\ &= (0)(0) \\ &= 0\end{aligned}$$


AND Logic Symbol

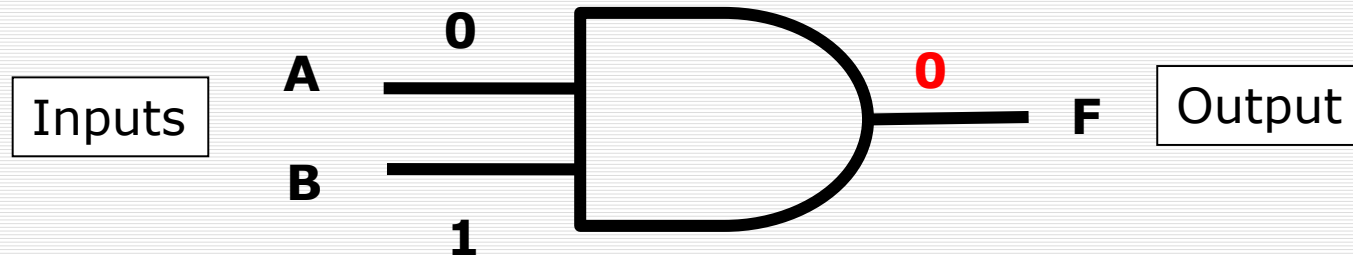

Determine the output

$$\begin{aligned}\text{Boolean Function : } F &= AB \\ &= (0)(1) \\ &= 0\end{aligned}$$

AND Logic Symbol

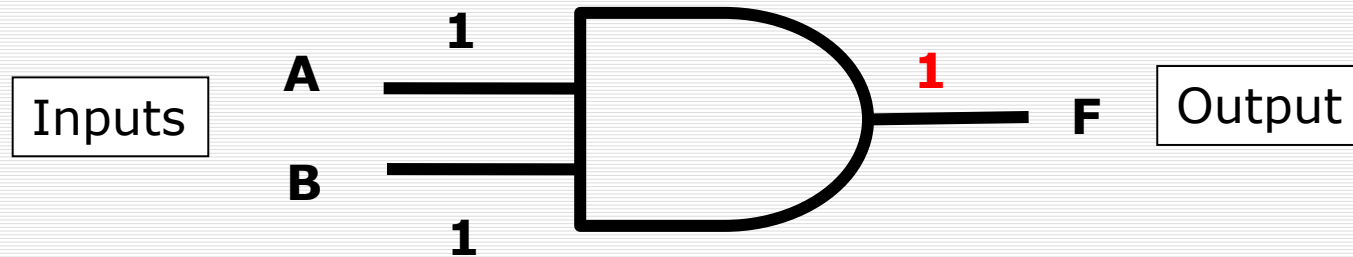

Determine the output

$$\begin{aligned}\text{Boolean Function : } F &= AB \\ &= (1)(1) \\ &= \mathbf{1}\end{aligned}$$

AND Truth Table

- ◇ To help understand the function of a digital device, a Truth Table is used:



Every possible
input combination

Input		Output
0	0	0
0	1	0
1	0	0
1	1	1

AND Function

AND Gates

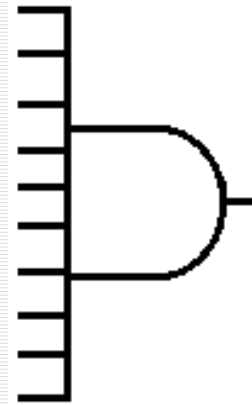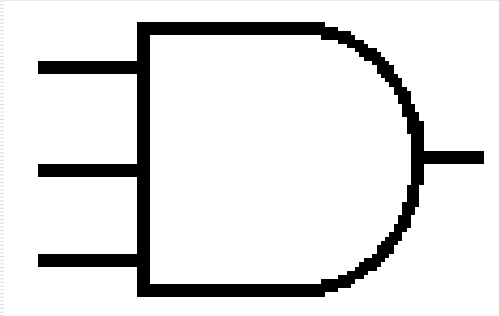- ◇ **It is possible to have AND gates with more than 2 inputs. The same logic rules apply – “if any input...”**




The OR Gate

- ◇ **The OR function:**
 - ◇ **if any input is high, the output is high**
 - ◇ **if all inputs are low, the output is low**

OR Logic Symbol


Boolean Function : $F = A + B$

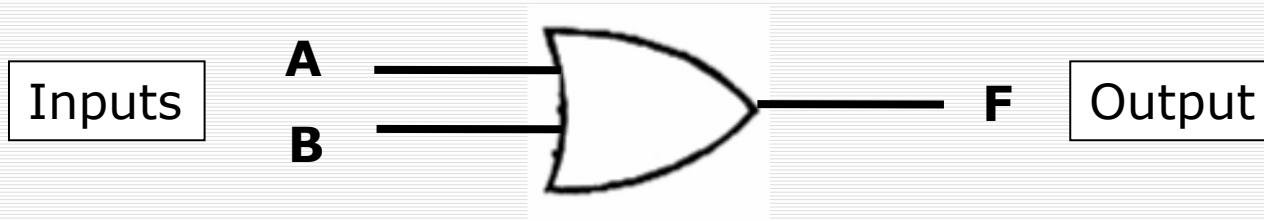

If any input is 1, the output is 1

If all inputs are 0, the output is 0


OR Logic Symbol

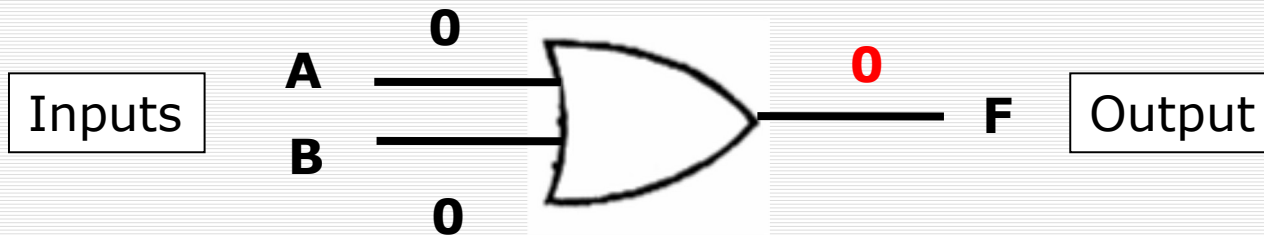

Determine the output

$$\begin{aligned}\text{Boolean Function : } F &= A+B \\ &= 0 + 0 \\ &= 0\end{aligned}$$


OR Logic Symbol

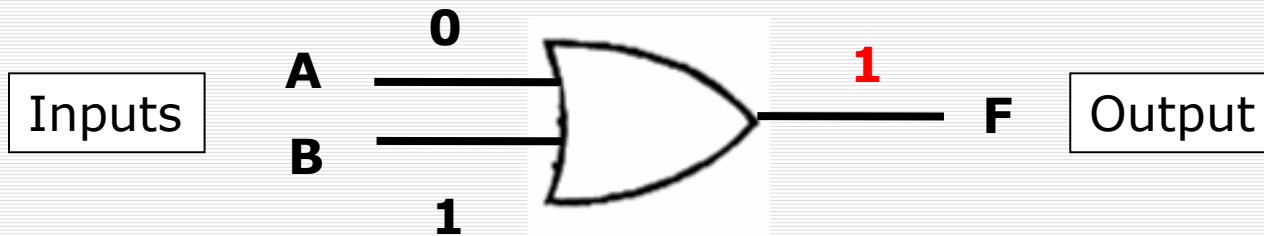

Determine the output

$$\begin{aligned}\text{Boolean Function : } F &= A + B \\ &= 0 + 1 \\ &= 1\end{aligned}$$

OR Logic Symbol

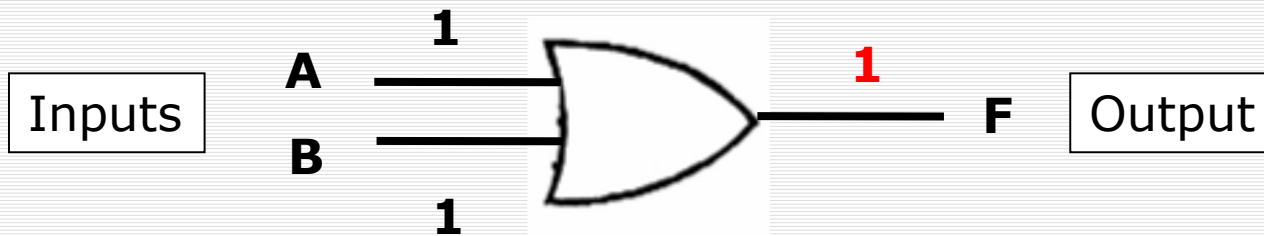

Determine the output

$$\begin{aligned}\text{Boolean Function : } F &= A + B \\ &= 1 + 1 \\ &= 1\end{aligned}$$

OR Truth Table

◇ Truth Table

Input		Output
0	0	0
0	1	1
1	0	1
1	1	1


OR Function

The NOT Gate

- ◇ **The NOT function:**
 - ◇ **If any input is high, the output is low**
 - ◇ **If any input is low, the output is high**
- ◇ **“The output is the opposite state of the input”**
- ◇ **The NOT function is often called INVERTER**

NOT Logic Symbol


Boolean Function : $F = A'$

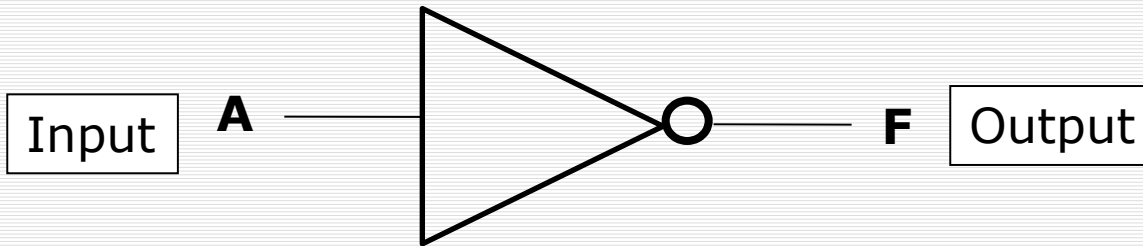

If the input is 1, the output is 0

If the input is 0, the output is 1


NOT Logic Symbol

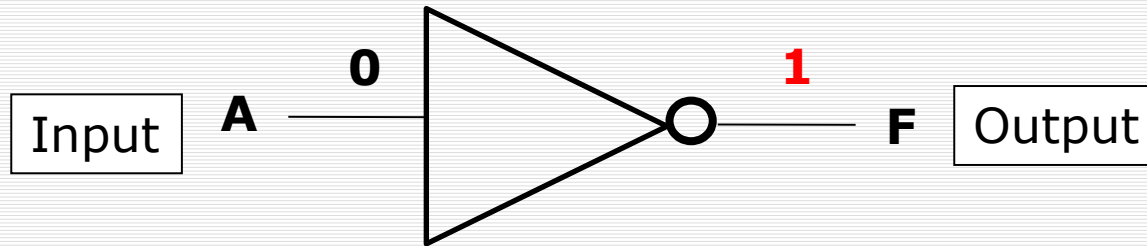

Determine the output

$$\begin{aligned}\text{Boolean Function : } F &= A' \\ &= (0)' \\ &= \mathbf{1}\end{aligned}$$

NOT Logic Symbol

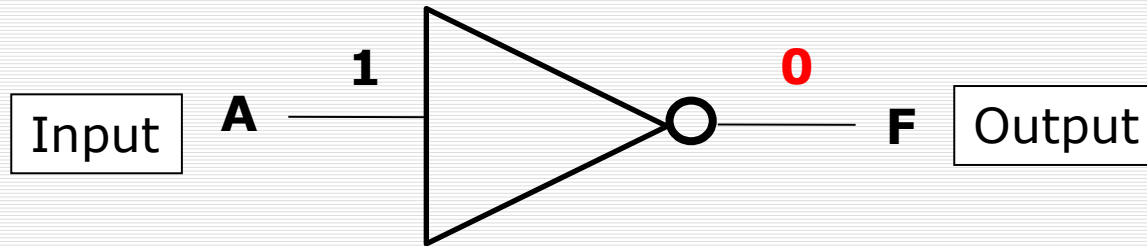

Determine the output

$$\begin{aligned}\text{Boolean Function : } F &= A' \\ &= (1)' \\ &= 0\end{aligned}$$

NOT Truth Table





◇ Truth Table

Input	Output
0	1
1	0

NOT Function


n-input Gates

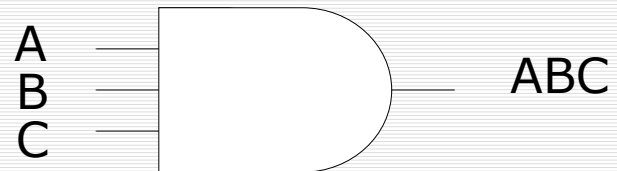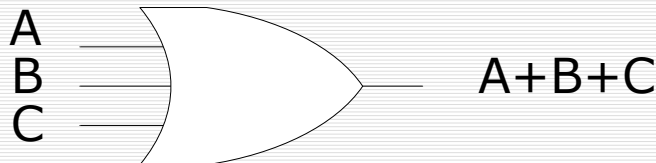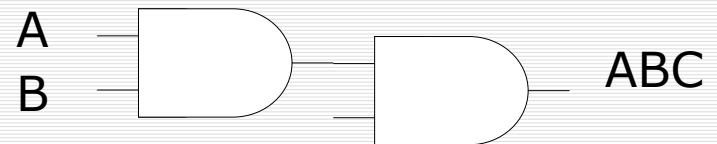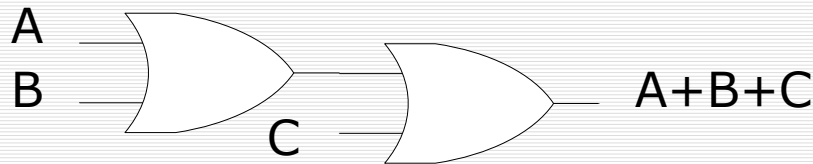- ◇ **Because + and * are binary operations, they can be cascaded together to OR or AND multiple inputs.**



n -bit Inputs

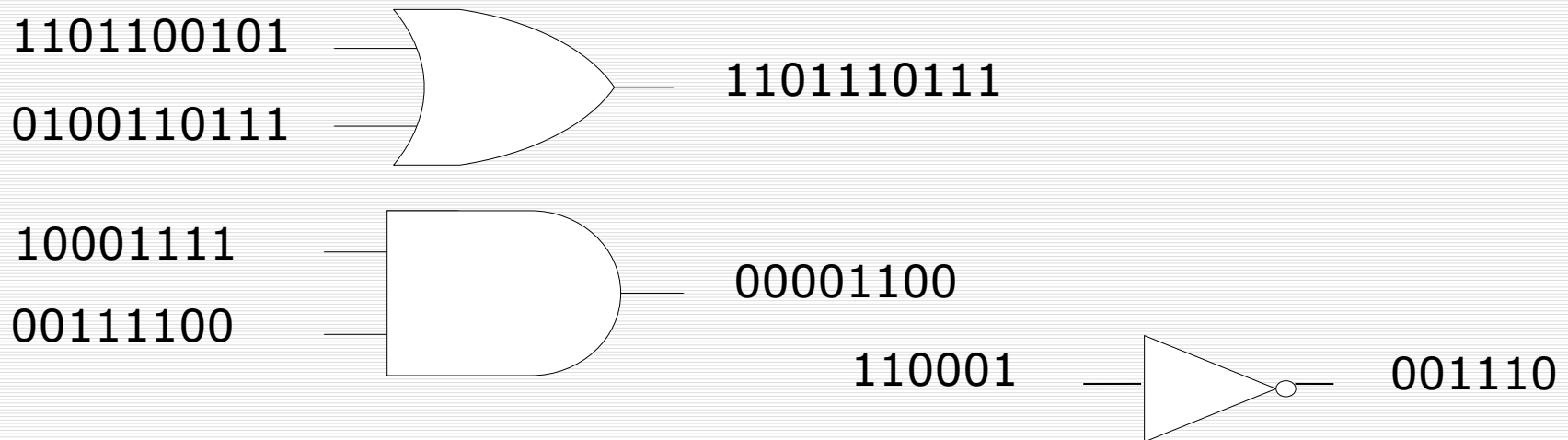- ◇ For convenience, it is sometimes useful to think of the logic gates processing n -bits at a time. This really refers to n instances of the logic gate, not a single logic gate with n -inputs.




The NAND Gate

- ◇ **The NAND function:**
 - ◇ **If all the inputs are high, the output is low**
 - ◇ **If any input is low, the output is high**

NAND Logic Symbol

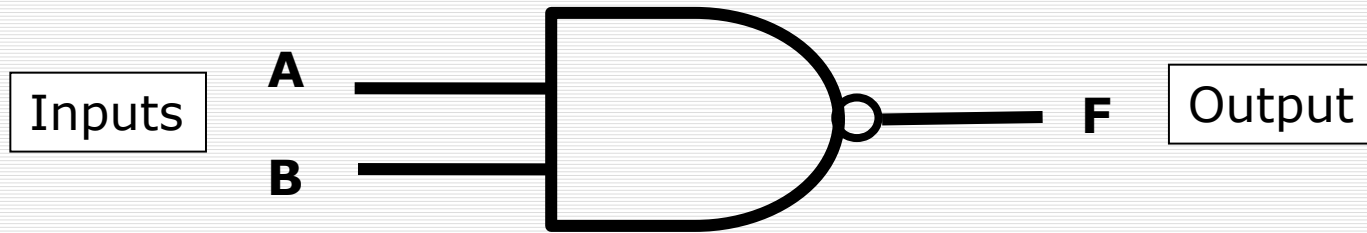
Boolean Function : $F = (AB)'$ or $F = \overline{AB}$



If any input is 0, the output is 1

If all inputs are 1, the output is 0


NAND Logic Symbol

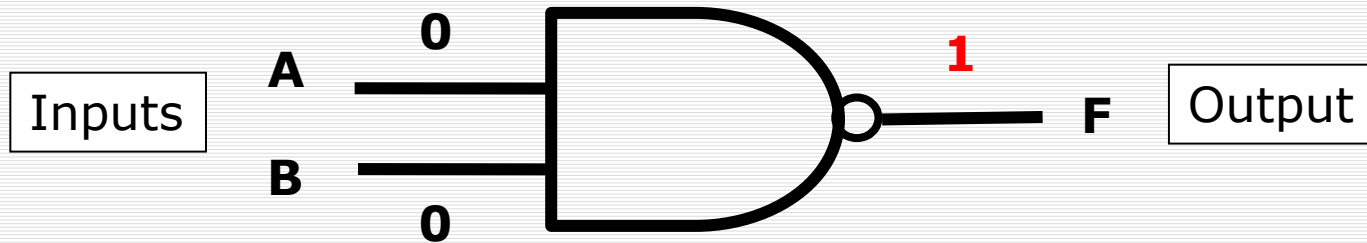

Determine the output

$$\begin{aligned}\text{Boolean Function : } F &= (AB)' \text{ or } F = \overline{AB} \\ &= [(0)(0)]' \\ &= (0)' \\ &= \mathbf{1}\end{aligned}$$


NAND Logic Symbol

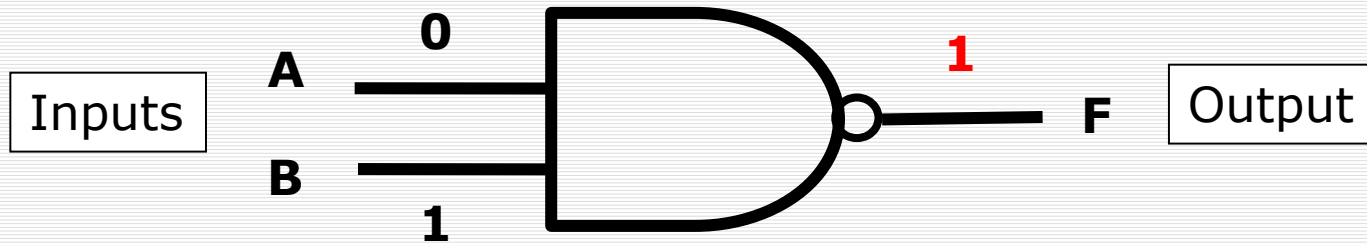

Determine the output

$$\begin{aligned}\text{Boolean Function : } F &= (AB)' \text{ or } F = \overline{AB} \\ &= [(0)(1)]' \\ &= (0)' \\ &= \mathbf{1}\end{aligned}$$

NAND Logic Symbol

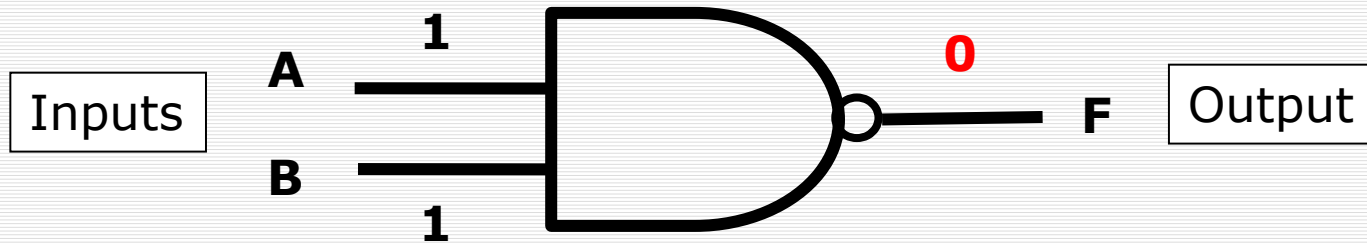

Determine the output

Boolean Function : $F = (AB)'$ or $F = \overline{AB}$

$$\begin{aligned} &= [(1)(1)]' \\ &= (1)' \\ &= 0 \end{aligned}$$

NAND Truth Table

◇ Truth Table

Input		Output
0	0	1
0	1	1
1	0	1
1	1	0


NAND Function

The NOR Gate

- ◇ **The NOR function:**
 - ◇ **If all the inputs are low, the output is high**
 - ◇ **If any input is high, the output is low**

NOR Logic Symbol

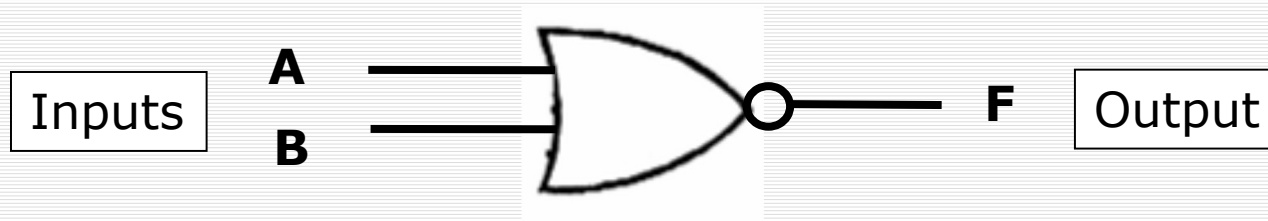
Boolean Function : $F = (A+B)'$ or $F = \overline{A+B}$



If any input is 1, the output is 0

If all inputs are 0, the output is 1


NOR Logic Symbol

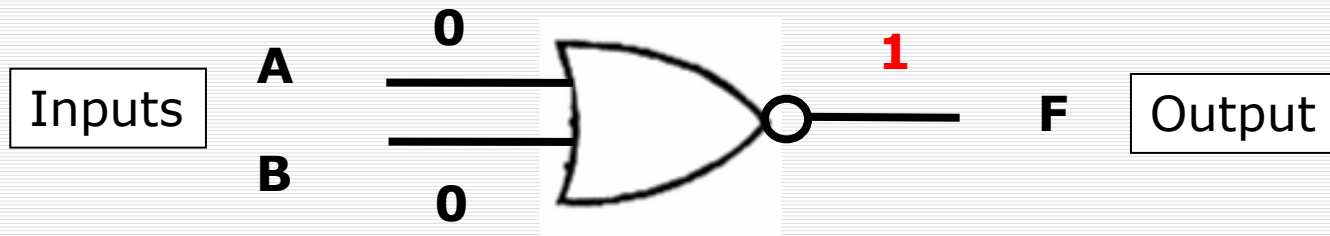

Determine the output

$$\begin{aligned}\text{Boolean Function : } F &= (A+B)'\text{ or } F = \overline{A+B} \\ &= [(0)+(0)]' \\ &= (0)' \\ &= \mathbf{1}\end{aligned}$$


NOR Logic Symbol

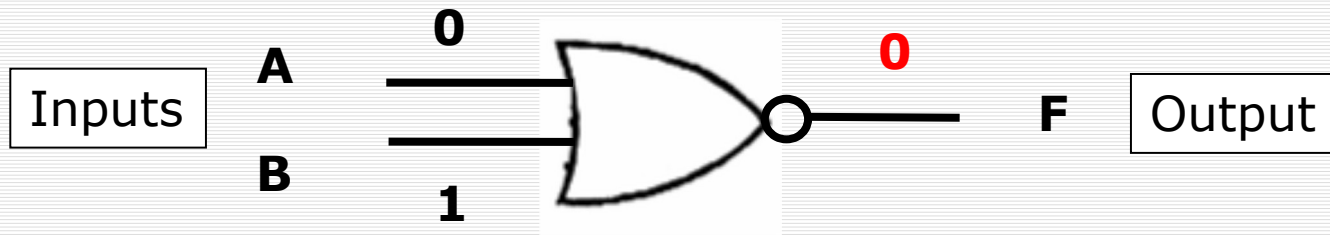

Determine the output

$$\begin{aligned}\text{Boolean Function : } F &= (A+B)' \text{ or } F = \overline{A+B} \\ &= [(0)+(1)]' \\ &= (1)' \\ &= 0\end{aligned}$$

NOR Logic Symbol

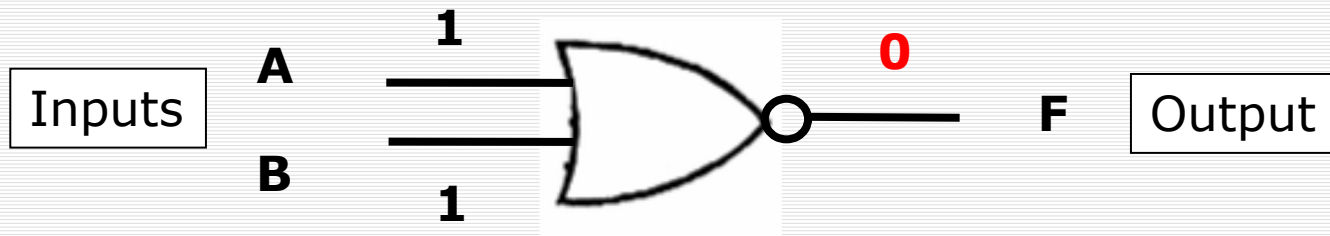

Determine the output

$$\begin{aligned}\text{Boolean Function : } F &= (A+B)' \text{ or } F = \overline{A+B} \\ &= [(1)+(1)]' \\ &= (1)' \\ &= 0\end{aligned}$$

NOR Truth Table

◇ Truth Table

Input		Output
0	0	1
0	1	0
1	0	0
1	1	0


NOR Function

The XOR Gate

- ◇ **The XOR function:**
 - ◇ **If either, but not both of its two inputs are high or low, the output is high**
 - ◇ **If all inputs are high or all input are low, the output is low**

XOR Logic Symbol


Boolean Function : $F = (A \oplus B)$

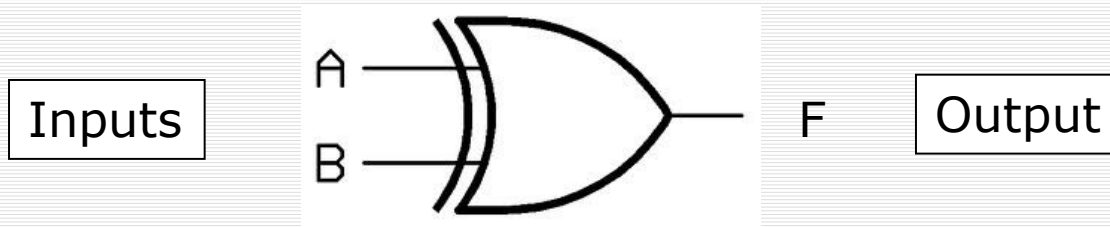

If any input is 1 or 0, the output is 1

If all inputs are 0 or 1, the output is 0


XOR Logic Symbol

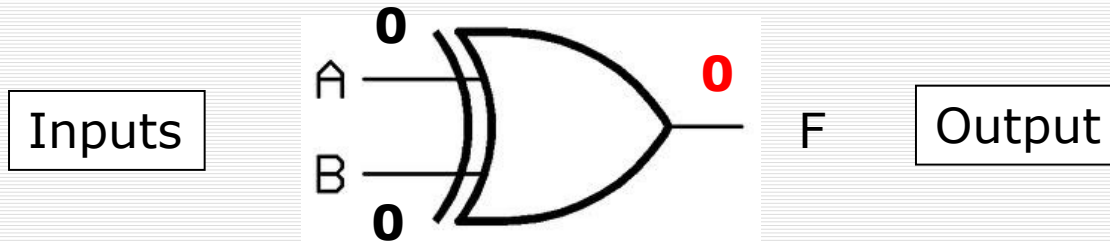

Determine the output

$$\begin{aligned}\text{Boolean Function : } F &= (A \oplus B) \\ &= (0 \oplus 0) \\ &= 0\end{aligned}$$


XOR Logic Symbol

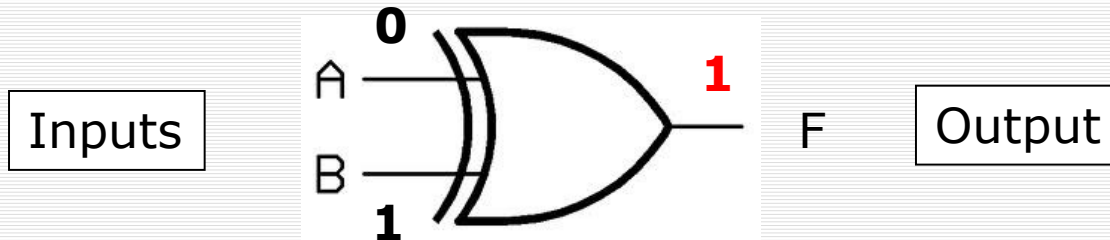

Determine the output

$$\begin{aligned}\text{Boolean Function : } F &= (A \oplus B) \\ &= (0 \oplus 1) \\ &= 1\end{aligned}$$

XOR Logic Symbol

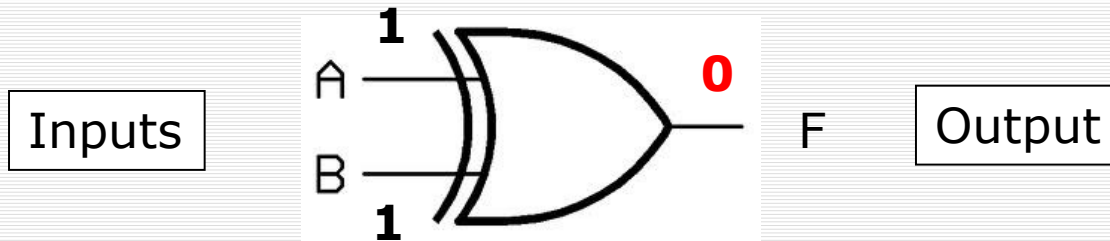

Determine the output

$$\begin{aligned}\text{Boolean Function : } F &= (A \oplus B) \\ &= (1 \oplus 1) \\ &= 0\end{aligned}$$

XOR Truth Table

◇ Truth Table

Input		Output
0	0	0
0	1	1
1	0	1
1	1	0


XOR Function

The XNOR Gate

- ◇ **The XNOR function:**
 - ◇ **If either, but not both of its two inputs are high or low, the output is low**
 - ◇ **If all input are high or all input are low, the output is high**

XNOR Logic Symbol


Boolean Function : $F = (A \oplus B)'$

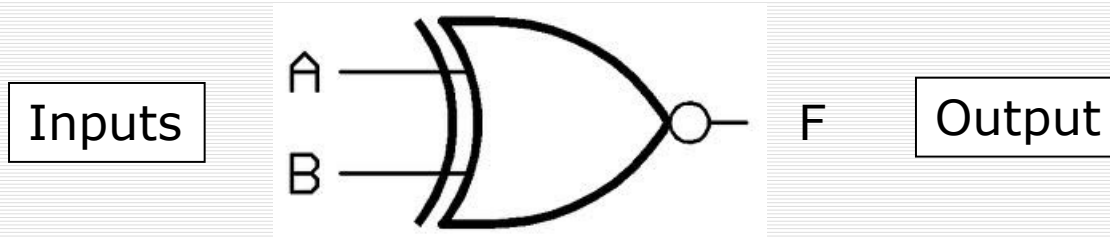

If any input is 1 or 0, the output is 0

If all inputs are 0 or 1, the output is 1


XNOR Logic Symbol

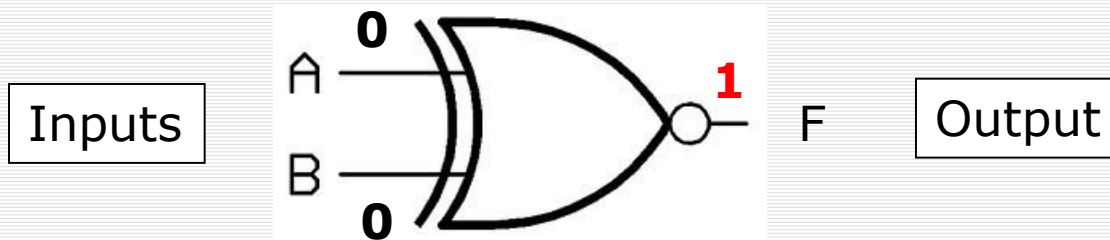

Determine the output

$$\begin{aligned}\text{Boolean Function : } F &= (A \oplus B)' \\ &= (0 \oplus 0)' \\ &= 1\end{aligned}$$


XNOR Logic Symbol

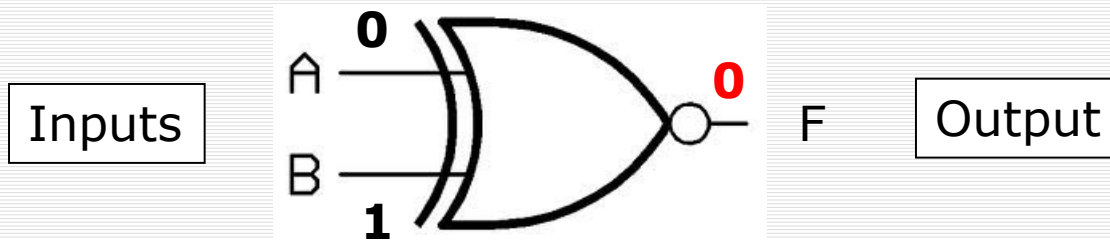

Determine the output

$$\begin{aligned}\text{Boolean Function : } F &= (A \oplus B)' \\ &= (0 \oplus 1)' \\ &= 0\end{aligned}$$

XNOR Logic Symbol

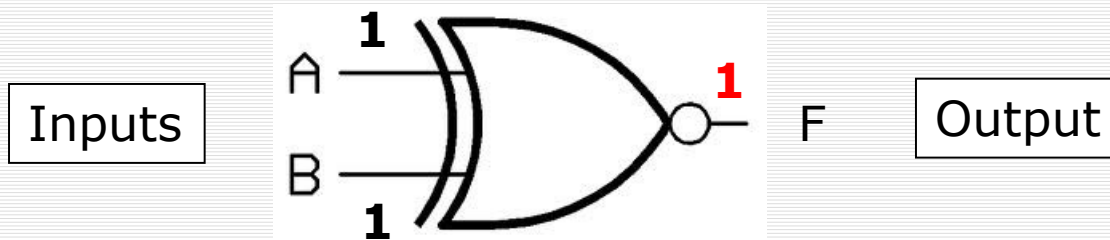

Determine the output

$$\begin{aligned}\text{Boolean Function : } F &= (A \oplus B)' \\ &= (1 \oplus 1)' \\ &= 1\end{aligned}$$

XNOR Truth Table

◇ Truth Table

Input		Output
0	0	1
0	1	0
1	0	0
1	1	1

XNOR Function

REVIEW

- ◇ **Digital Electronics works in Binary:**
 - ◇ **There are 2 logic levels: high and low, or 1 and 0.**
 - ◇ **A switch can be used to provide a logic level.**

Exercise 1

- ◇ **Complete the sentences:**
 - ◇ **If all inputs of an OR gate are low, the output is _____**
 - ◇ **If any input of an AND gate is low, the output is _____**
 - ◇ **The output of a NOT gate is always the _____ of the input.**