

What is encoder and decoder ?

- The combinational circuits that modify the binary data into N output lines are known as Encoders. The combinational circuits that convert the binary data into $2N$ output lines are called Decoders.